

**Zeal Education Society's
Zeal College of Engineering & Research, Pune
Department of Electronics and Computer Engg**

Subject : Basic Electronics Engg

Name of Staff: Dr. Mahesh Navale

Unit II : Semiconductor Materials

- Semiconductors: P-type and N-type, Current in semiconductors: Diffusion and Drift Current.
- P-N Junction Diode: Construction, working in forward and reverse bias, V-I characteristics, Diode applications: Diode as a switch, Diode as Rectifier: HWR, FWR, BR, Specifications of Rectifier diodes.
- Special purpose diodes: Zener diode: V-I Characteristics, Specification and Zener as voltage regulator, Light Emitting Diode (LED) and photo diode.

Intrinsic Semiconductor :


Pure form of semiconductor

Current flows due to excitation of electrons
Reason behind this is temperature, heat, light etc.

Very less free electrons $\therefore$ ct. is less, called as "leakage ct"

Comparatively silicon is having less leakage ct. than Germanium

Fig shows ~~the~~ Atomic structure of Intrinsic spc

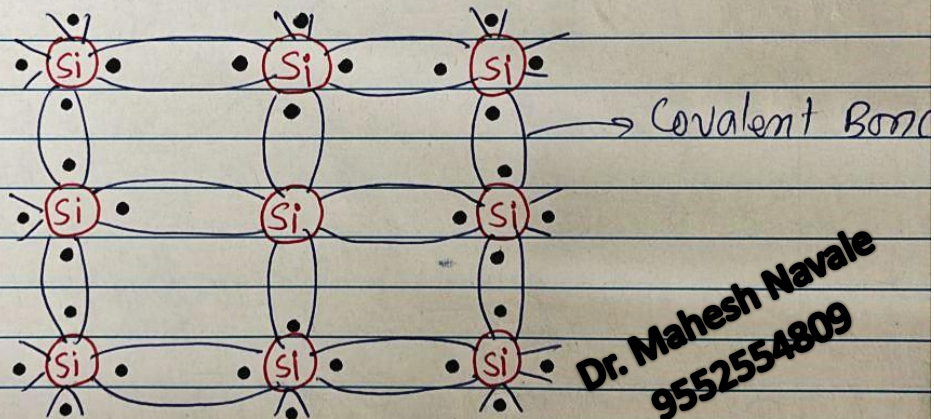

Dr. Mahesh Navale
 9552554809

Here covalent bond is formed between two silicon Silicon atom itself.

To balance, it must consist of 8 electrons in its outermost orbit

Thus due to covalent bond, now each silicon consists of 8 electrons in its outer most orbit & becomes balance

When any external energy such as temp,

light & etc is applied, these electrons become free due to which current flows through it.

Furthermore if an external source is applied, due to ~~moment~~ movement of electrons, current flows through semiconductor.

Dr. Mahesh Navale
9552554809

* Extrinsic Semiconductor

It is impure form of semiconductor
It is formed by adding impurities to pure semiconductor

The process of adding impurity is called as "Doping"

Based on impurity added, there are two types of extrinsic semiconductor

- P type -||-
- N type -||-

Dr. Mahesh Navale
9552554809


① P Type Semiconductor :

Here a trivalent impurity is added with pure semiconductor

These trivalent impurities are also called as "Acceptor Impurities"

An ~~exa~~ example of trivalent impurity is -
Gallium, Indium & etc.

fig shows formation of P-type slc

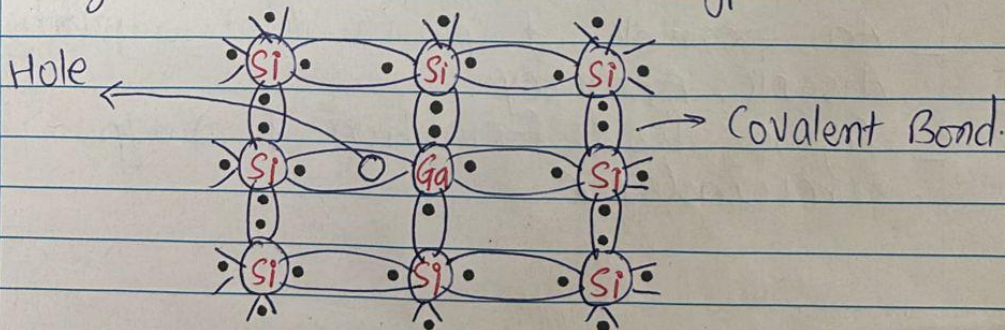

- Due to addition of trivalent impurity, large no. of holes are created in semiconductor
Here covalent bond is formed between pure semiconductor & an impurity

- Thus it will be balanced due to addition of hole

where hole is a positive charged carrier
And it represents a missing of electron
As trivalent impurity has only 3 electrons in its outermost orbit, covalent bond is formed with the help of hole.

- In P type semiconductor, holes are majority carriers whereas electrons are minority carriers

2) N-Type Semiconductor


Dr. Mahesh Navale
9552554809

- Here a pentavalent impurities are added with pure semiconductor.

- These pentavalent impurities are also called as "Donor impurities"

- An example of pentavalent impurity is Arsenic, Antimony.

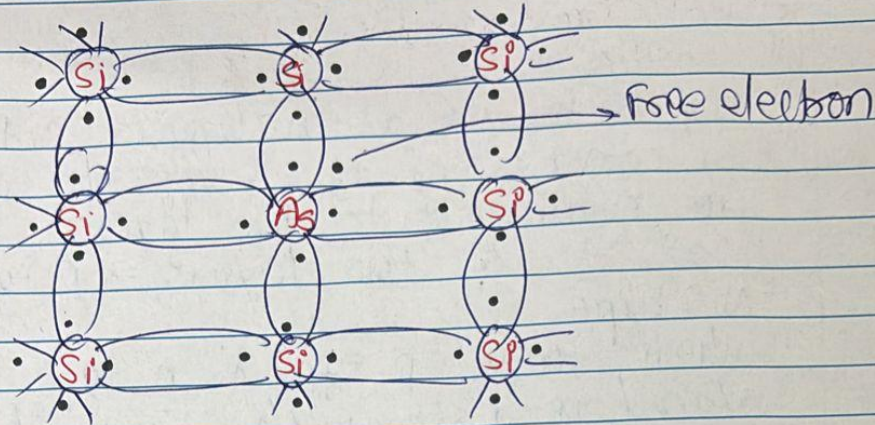- Figure shows formation of n-type semiconductor



Due to addition of pentavalent impurity, large no. of free electrons are created.

As pentavalent impurity has 5 electrons in its outermost orbit, 4 electrons of them form a covalent bond with 4 electrons of pure semiconductor and becomes balance.

But the 5th electron of impurity doesn't form any bond & thus becomes free electron.

As it has large no. of electrons, in N type semiconductor, electrons are majority carriers where as holes are minority carriers.

Dr. Mahesh Navale
9552554809

* PN Junction Diode

1) construction / structure :


Diode is an abbreviation of **Di-Electrode**.
 It consists of two electrodes which are connected to two layers.

Thus it has two layers - P type & N-type

When these p type & n type slc placed near to each other, It forms a junction


Thus diode is a Unijunction device when p type & n type slc placed together, at the junction due to repulsion of majority carriers, a depletion layer is formed.

figure shows structure of P-N junction diode

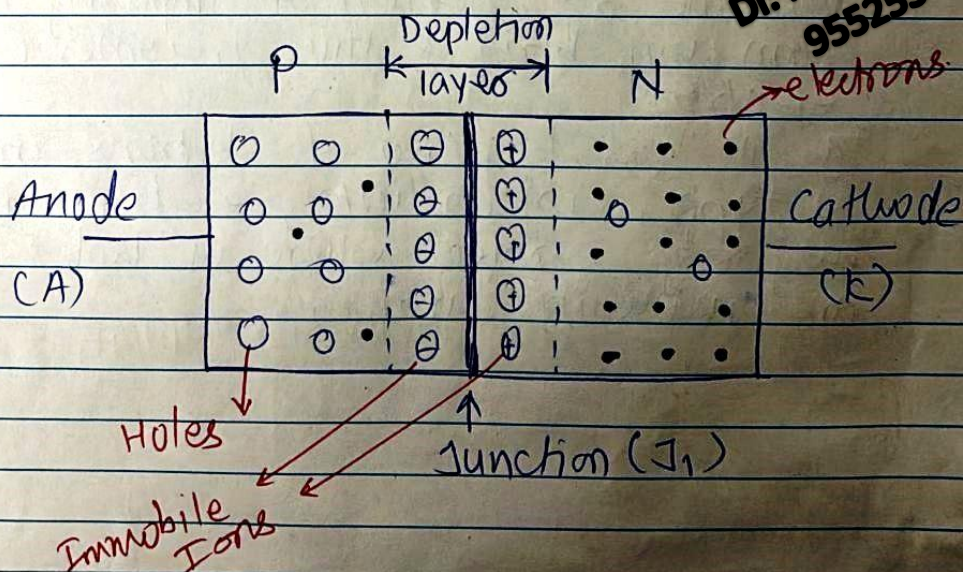

Dr. Mahesh Navale
 9552554809

The symbol PN junction diode is —

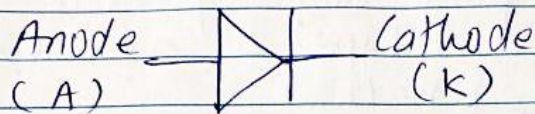

2) Working Principle | V-I characteristics $\Rightarrow$


Diode basically works in two different conditions

- 1) Forward Bias Condition
- 2) Reverse Bias condition

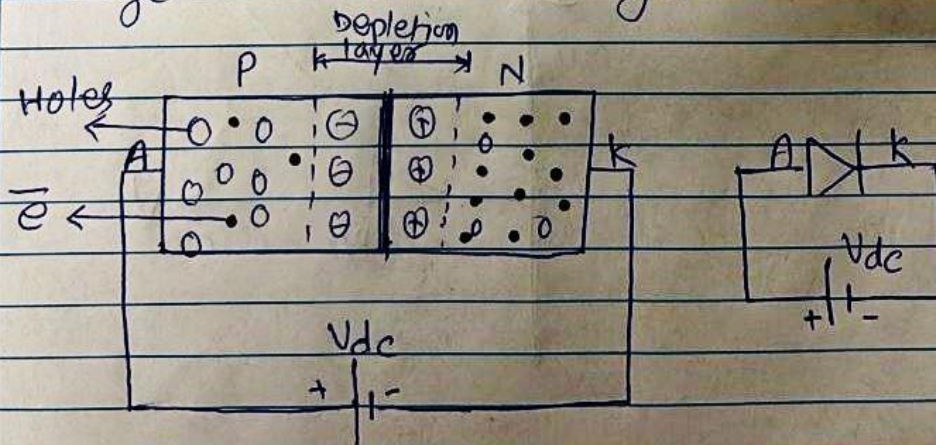1) Forward Bias condition

Dr. Mahesh Navale
9552554809

Here P type material (Anode) is connected to positive plate of supply voltage & N type material (Cathode) is connected to negative plate of supply voltage as shown in figure



When external DC voltage is applied, due to +ve plate, majority carriers (holes) from P type $\bullet$ gets repelled towards the junction.

Similarly due to -ve plate of the supply voltage, electrons from N type gets repelled towards junction.


Due to this, the junction barrier decreases.

When the supply voltage is further increased, one state will come at that time the junction barrier collapse & heavy current flows through diode.

This current is called as forward ct.

And the voltage at which junction breaks, called as Break Over voltage.


Figure shows V-I characteristics in forward bias condition.

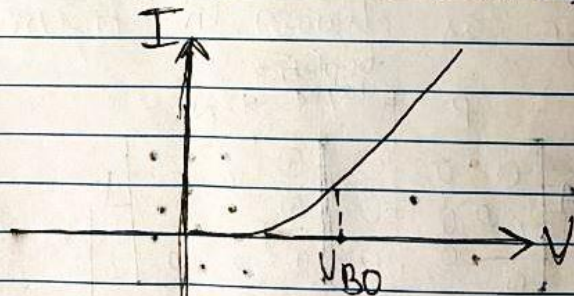

Dr. Mahesh Navale
9552554809

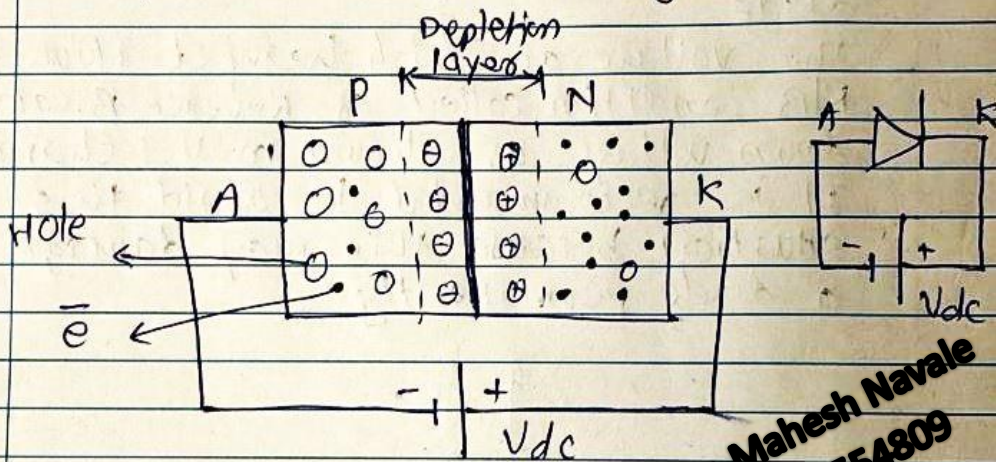2) Reverse Bias Condition

Here P type material (Anode) is connected to -ve plate of supply voltage & N type material (Cathode) is connected to +ve plate as shown in figure



Dr. Mahesh Navale
 9552554809

When external DC voltage is applied, due to the terminals, majority carriers from P type (Hole) & ~~electrons~~ N type (electrons) gets attracted towards DC source

Due to this, junction barrier increases. At the same time, minority carriers may be able to cross the junction, resulting in flow of small amount of current.


This current is called as leakage current.

- When the reverse supply voltage is further increased, an existing covalent bond will break creating large no. of minority carriers.

- Due to this heavy current flows through diode


- The voltage at which heavy ct. flows in RLB condition called as Reverse Break-down voltage as shown in V-I chara.

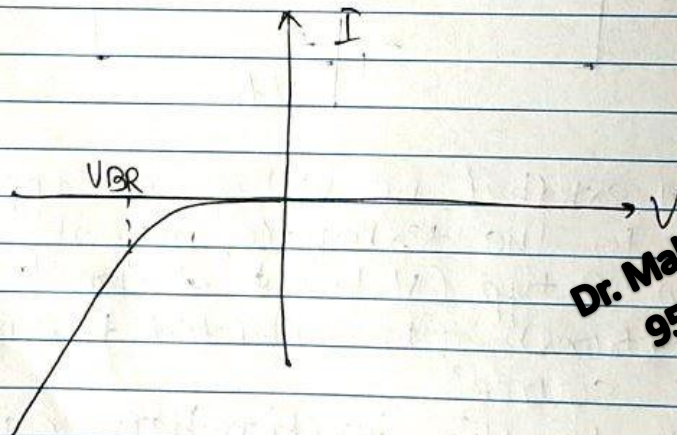- It is recommended to avoid this situation because this may damage a diode permanently.



Dr. Mahesh Navale
9552554809

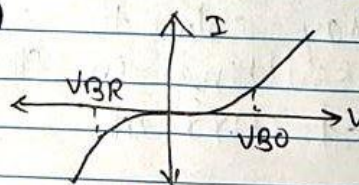- Fig. shows V-I chara of diode both in F/W & RLB condition



* Applications of Diode

1) Diode as a Rectifier

Rectifier is basically used to convert bidirectional $\sin$ signal (AC) to unidirectional $\sin$ signal (DC)

Based on the output, there are basic two types of Rectifiers.

Dr. Mahesh Navale
9552554809

Half wave Rectifier

Full wave Rectifier

Full wave Centre Tap Rectifier

Full wave Bridge Rectifier

* Half wave Rectifier

Here only one diode is connected in series with load resistance (R_L) as shown in figure 1

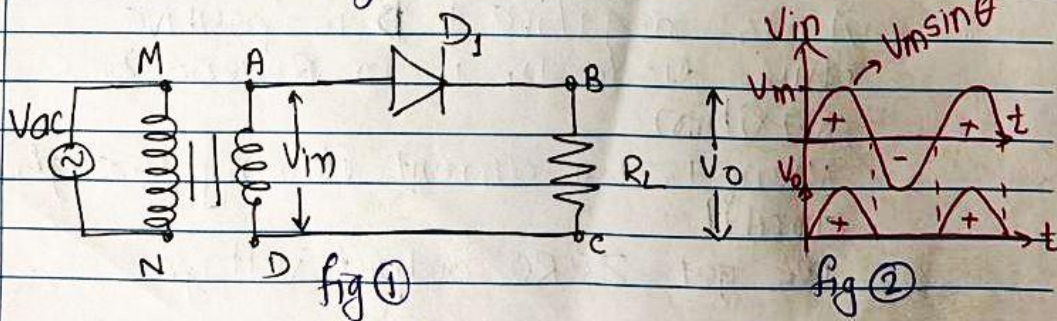


Figure 2 shows input, output waveforms.

The working of the circuit is explained with the help of two different conditions of applied i/p cycle.

1) For Positive Half Cycle.

Dr. Mahesh Navale
9552554809

M is positive with respect to N.

A is positive with respect to D.

Thus diode D_1 is in forward bias condition.

Current flows through the circuit as -

$A - D_1 - B - R_L - C - D$

Thus current flowing through R_L is from B to C ($R_L \downarrow$)

Let us consider that this current produces positive o/p voltage. $\therefore V_o = +ve$

2) For Negative Half Cycle.

M is negative & N is positive.

A is negative & D is positive.

Thus diode D_1 is in Reverse bias condition.

There is no current flowing through circuit.

We get ZERO output voltage.

• Thus only for +ve Half cycle we get o/p $\therefore$ HWR.

* Centre Tap Full wave Rectifier.

Here a transformer which consists of a centre tapping at its secondary winding is used.

Here two diodes are used as shown in figure 1

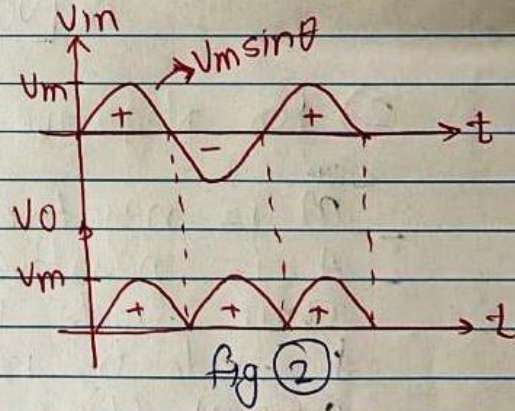
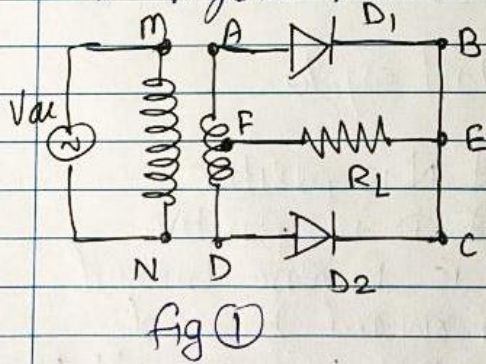


Figure 2 shows input, output waveforms.

* Working

1) For Positive Half Cycle

M is positive w.r. to N.

A is positive w.r. to D.

Thus diode D_1 is forward biased &
 D_2 is Reverse biased.

Current flows through the circuit as -

A - D_1 - B - E - R_L - F

Thus current flowing through R_L
is from E to F ($\overleftarrow{R_L}$)

Let us consider that this current
produces positive o/p voltage

$$\therefore \boxed{V_o = +ve}$$

2) For Negative Half cycle

M is negative & N is positive

A is negative & D is positive

Thus diode D_1 is Reverse biased
& diode D_2 is forward biased.

Current flows through the circuit as -

D - D_2 - C - E - R_L - F

Thus current flowing through R_L
is from E to F ($\overleftarrow{R_L}$)

Dr. Mahesh Navale
9552554809

And as we already assumed that if current flowing through R_L is from E to F, positive o/p voltage is produced

$$\therefore [V_o = +V_e]$$

Thus, here both the half cycles of applied i/p, generates +ve o/p $\therefore$ it is called as FWR.

Dr. Mahesh Navale
9552554809

* Bridge Rectifier

Here four diodes are used in a bridge form as shown in fig. 1

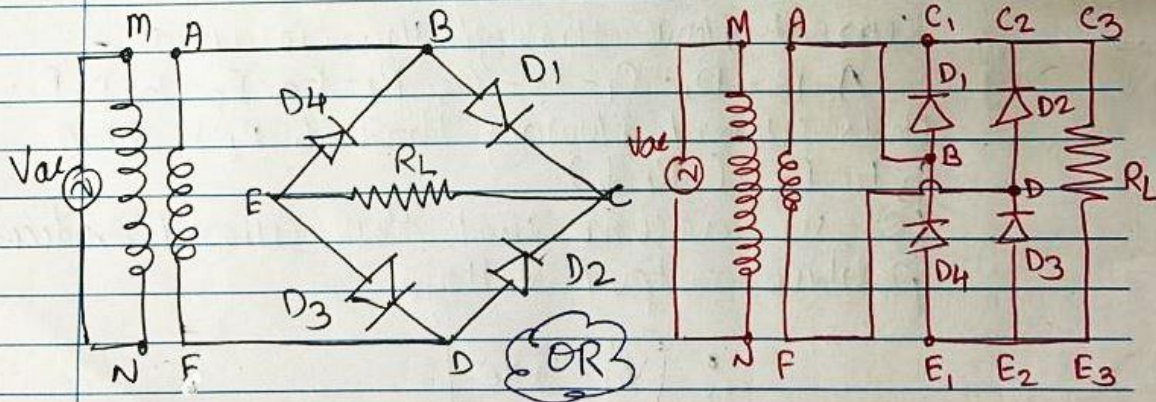


fig 1 (a)

$$C = C_1 = C_2 = C_3$$

$$E = E_1 = E_2 = E_3$$

fig 1 (b)

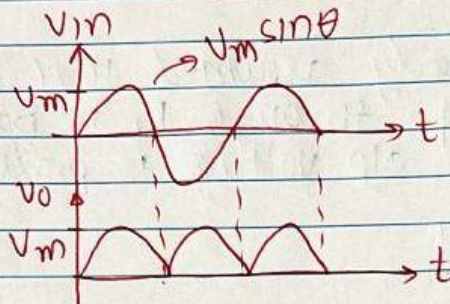


Fig 2 shows
input, output
waveforms.

Working (With Reference to Fig 1b)

1) for Positive Half Cycle

- M is positive w.r to N

- A is positive w.r to F

- Thus B is positive w.r to D.

- Due to this diodes D_1 & D_3 becomes forward biased and diode D_2 & D_4 becomes reverse biased.

- Current flows through the circuit as -

A-B- D_1 -C- C_2 - C_3 - R_L -E₃-E₂- D_3 -D-F.

Thus current flowing through R_L is from C_3 to E₃ ($R_L \downarrow$)

- Let us assume that this current produces positive output voltage

$$\therefore \boxed{V_o = +ve}$$

Dr. Mahesh Navale
9552554809

2) for Negative Half Cycle

M is negative, N is positive

A is negative, F is positive

B is negative, D is positive

Due to this diodes D_2 & D_4 becomes forward biased whereas diodes D_1 & D_3 reverse biased.

Current flows through the circuit as -

F - D - D_2 - C_2 - C_3 - R_L - E_3 - E_2 - E_1 - D_4 - B - A

Thus current flowing through R_L is from C_3 to E_3 (R_L)

As the current flowing through R_L produces positive o/p voltage, we get,


$$V_o = +ve$$

Thus, here both the input half cycles are converted into positive so as to get positive output voltage.

Dr. Mahesh Navale
9552554809

* Diode as a Switch


Case 1) Switch ON condition

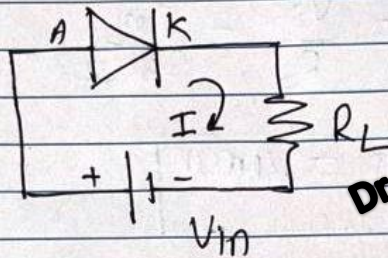

Dr. Mahesh Navale
9552554809

- Here, diode is in forward bias condition & turns ON.
- Current flows through circuit & we get output across load.
- This is a switch 'ON' condition.

Case 2) Switch OFF condition

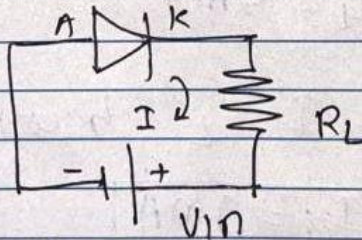


Dr. Mahesh Navale
9552554809

- Here diode is in reverse bias condition & remain in cut off state.
- There is no current flowing through circuit & thus we have zero o/p voltage.
- This is switch 'Off' condition.

* Diode as a protection device

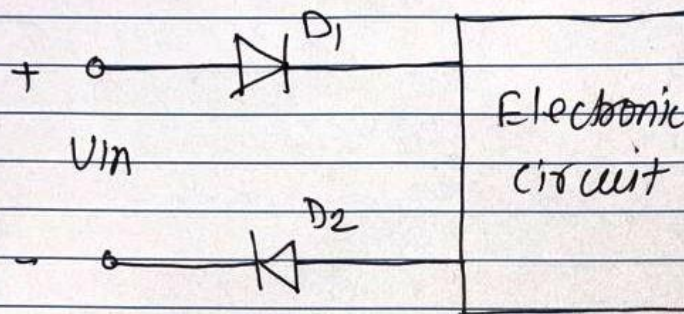- It is basically used for the protection of circuit from supply reversal. as shown below




- When the supply voltage is connected properly, both the diodes become forward bias.
- This will source the circuit.
- When supply voltage gets reversed, both diodes become reverse biased.
- Thus protecting an electronic circuit.


Dr. Mahesh Navale
9552554809

* Zener Diode

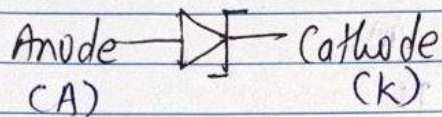- It is a special purpose diode.
- It operates in reverse bias condition.
- It is heavily doped to reduce reverse breakdown voltage
- The symbol of zener voltage is -



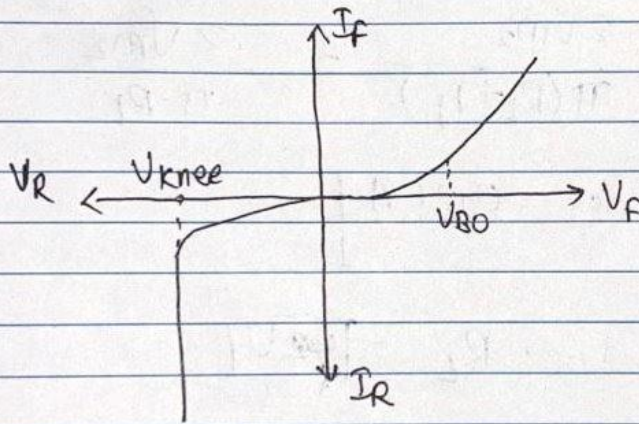- Zener diode has a sharp breakdown in R/B as shown in V-I characteristics




- For F/B condition, it behaves same as an ordinary diode.

* Zener Diode as a Voltage Regulator

Regulator is a device which keeps output voltage constant irrespective of change in input voltage and or load current.

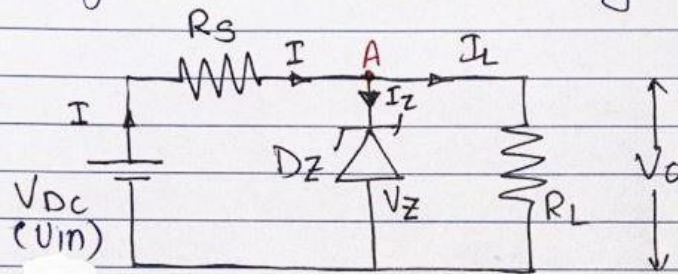Here zener diode is used as a vltg regulator as shown in fig.



As shown in figure, zener diode is connected across the load resistance.

The series resistance R_S is used for current limiting purpose.

As load is connected across zener,

$$\boxed{V_Z = V_L = V_O = \text{constant}}$$

The working of the circuit is explained with the help of two conditions.

Case 1) V_{in} is fixed & Variable R_L

(As R_L is variable, so as I_L)

- Here, so as to keep zener in ON state in reverse bias condition, one has to get (R_{Lmin} & I_{Lmax}) and (I_{Lmin} & R_{Lmax})

• for R_{Lmin} & I_{Lmax}

- when R_L is minimum, I_L is maximum.

$$\therefore I_L = \frac{V_0}{R_L}$$

- But $V_0 = V_Z = V_L$ (from fig)

$$\therefore V_0 = \frac{V_{in} \cdot R_L}{R_S + R_L}$$

$$\therefore R_L = \frac{R_S \cdot V_Z}{V_{in} - V_Z} \quad (\because V_0 = V_Z)$$

$$\therefore \boxed{R_{Lmin} = \frac{R_S \cdot V_Z}{V_{in} - V_Z}}$$

$$\text{But } I_L = \frac{V_0}{R_L} = \frac{V_Z}{R_L} \therefore \boxed{I_{Lmax} = \frac{V_Z}{R_{Lmin}}}$$

- for I_{Lmin} & R_{Lmax}

from fig. Apply KCL at A

$$\therefore I = I_Z + I_L$$

$$\therefore I_Z = I - I_L$$

$$\& I_L = I - I_Z$$

$$\therefore \boxed{I_{Lmin} = I - I_{Zmax}}$$

& we have

$$V_0 = V_Z = V_L = I_L \cdot R_L$$

$$\therefore \boxed{R_{Lmax} = \frac{V_Z}{I_{Lmin}}}$$

Case 2) R_L is fixed & V_{in} is variable

(As R_L is fixed, so as I_L)

Here, to turn on zener, one has to get minimum & maximum value of V_{in} .

• for $V_{in}(\min)$

we have,

$$V_o = V_z = \frac{V_{in} \cdot R_L}{R_s + R_L}$$

$$\therefore V_{in}(\min) = \frac{(R_s + R_L) \cdot V_z}{R_L}$$

• for $V_{in}(\max)$

we have, $I = I_z + I_L$.

OR.

$$I_{\max} = I_{z\max} + I_L$$

Apply KVL to i/p loop, we get

$$V_{in} = I \cdot R_s + V_z \quad \therefore V_{in}(\max) = I_{\max} \cdot R_s + V_z$$

